



United International University
QUEST FOR EXCELLENCE



CSE 1326: Digital Logic Design Lab


3-Bit Binary to Gray code

United International University

What to do

- 1. Problem Description:** Find out the relation between 3-bit binary to gray code. The circuit will take a binary code as input, and provide the corresponding gray code as output.
- 2.** Derive the truth table from problem description.

	Binary A B C	Gray Code X Y Z
m0	0 0 0	0 0 0
m1	0 0 1	0 0 1
m2	0 1 0	0 1 1
m3	0 1 1	0 1 0
m4	1 0 0	1 1 0
m5	1 0 1	1 1 1
m6	1 1 0	1 0 1
m7	1 1 1	1 0 0

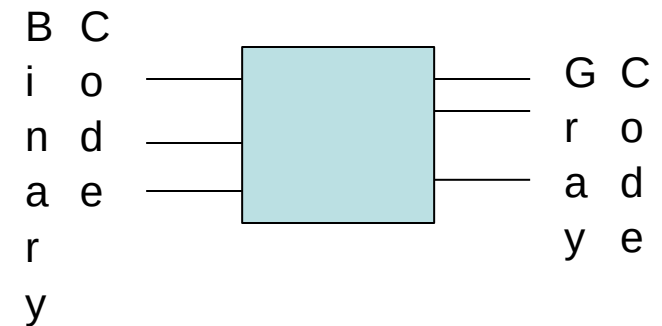

How to proceed

3. Now, derive the functions from Truth Table (TT)
 - $X = F(A, B, C) = ??? = \text{sum of minterms}$
 - $Y = F(A, B, C) = ??? = \text{sum of minterms}$
 - $Z = F(A, B, C) = ??? = \text{sum of minterms}$
4. Minimize/Optimize/Simplify functions: (Boolean algebra or Karnaugh Maps)
 - Draw K-map according to # of minterms
 - Populate 1's and 0's
 - Group 1's in the number of power of 2 using rectangles. The larger the rectangles, the better
 - Write function: You will get a term from each rectangle.

How to proceed

4. Build the circuit in LogiSim and Trainer board.
5. Verify the circuit according to the truth table.

Writing Report

- The report should contain the following:
 - Decimal and Binary representation of 3-Bit Gray code
 - The K-maps you have drawn and the minimized functions for X, Y and Z
 - The circuit diagram
 - List of ICs you used