



United International University
QUEST FOR EXCELLENCE




CSE 1326: Digital Logic Design Lab Counters with Arbitrary Sequences

United International University

Objective

- Implement an arbitrary sequence Counter using D and J-K flip-flop.
 - Count the following sequence repeatedly
 - 2->3->1->4->6->0->2->so on, Sec D, E, no class after in class assignment.
 - If accidentally the counter starts with '5' or '7', it should move to '0' in the next step

State Diagram

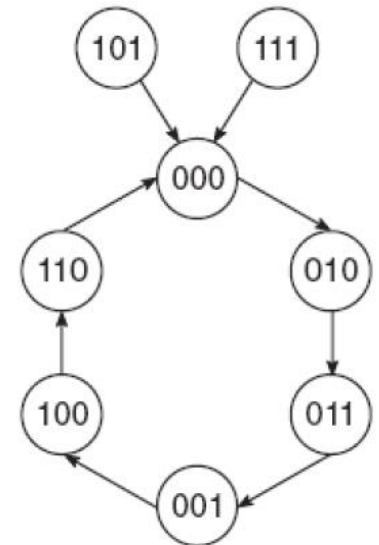

Flip-flop input table: using J-K

2->3->1->4->6->0->2->so on

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

J-K Excitation Table

Present state			Next state			Inputs					
			D ₂	D ₁	D ₀						
Q ₂	Q ₁	Q ₀	Q ₂	Q ₁	Q ₀	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
0	0	0	0	1	0	0	X	1	X	0	X
0	0	1	1	0	0	1	X	0	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	1	0	X	X	1	X	0
1	0	0	1	1	0	X	0	1	X	0	X
1	0	1	0	0	0	X	1	0	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	0	0	0	X	1	X	1	X	1

Input Equations

$$J_2 = Q_0 \cdot \overline{Q_1}$$

$$K_2 = Q_1 + Q_0$$

$$J_1 = \overline{Q_0}$$


$$K_1 = Q_2 + Q_0$$

$$J_0 = Q_1 \cdot \overline{Q_2}$$

$$K_0 = \overline{Q_1} + Q_2$$

Verify that you also have the same equations.

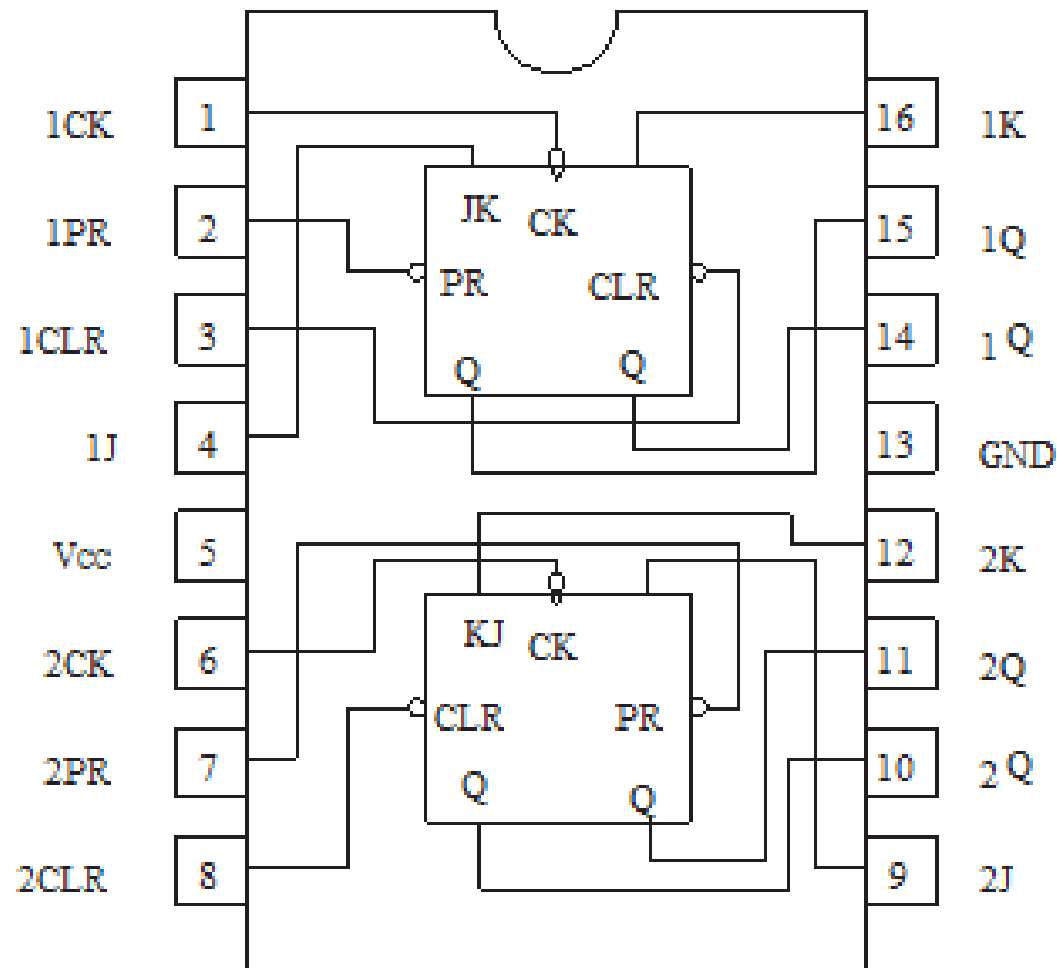74LS76AP: Dual J-K Flip-Flops (with Preset and Clear)



Writing Report

- ICs being used
- For the arbitrary sequence counter, provide for both J-K and D flip-flop
 - Flip-flop Input/Output (state) tables
 - K-maps
 - Equations
 - Circuit diagrams
- Answer the following questions:
 - How can you test the statement, “If the counter starts with ‘5’ or ‘7’, it should move to ‘0’ ?”